

PRE-LAB →

For Obj. 1 → Design a combinational circuit with four inputs A, B, C & D and one output F.

The output F value is 0 if three or four of the inputs are 1; otherwise the value of F is 1.

a) Truth table →


Inputs				Output
A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

b) Minimised Boolean Function →

AB \ CD				
	00	01	11	10
00	1	1	1	1
01	1	1	0	1
11	1	0	0	0
10	1	1	0	1

$$F_{max} = (B' + C' + D')(A' + C' + D')(A' + B' + C')(A' + B' + D')$$

c) Circuit Diagram →

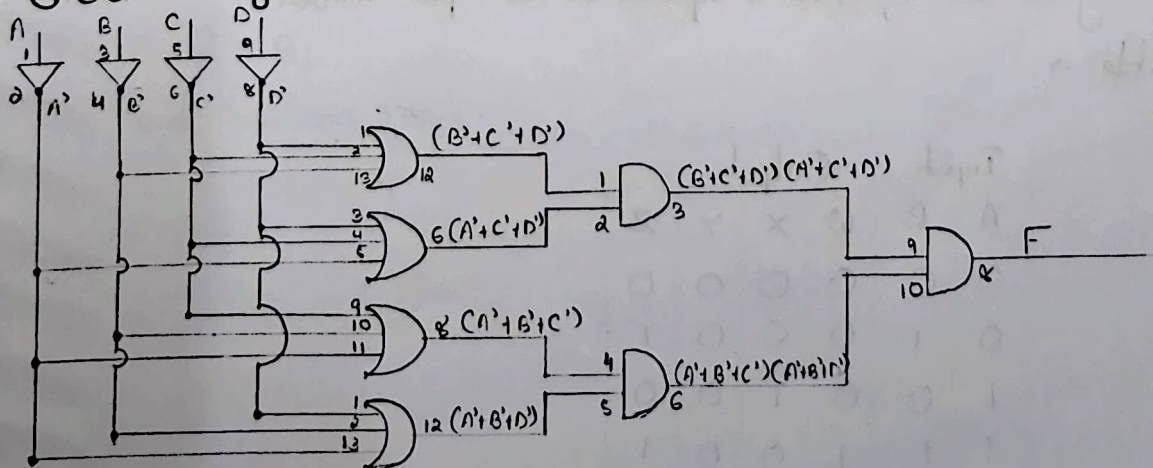

d) HDL code →

library ieee;

use ieee.std_logic_1164.all;

entity test10 is

port (A, B, C, D : in std_logic;

F : out std_logic);

end test10;

architecture boolean_eq of test10 is

signal a, b, c, d, e, f, g, h, i, j : std_logic;

Begin

a <= NOT A;

b <= NOT B;

c <= NOT C;

d <= NOT D;

e <= b OR c OR d;

f <= a OR c OR d;

g <= a OR b OR c;

h <= a OR b OR d;

i <= e AND f;

j <= g AND h;

F = i AND j;

end boolean_eq;

For Obj. 2 → Design a combinational circuit that accepts a 2-bit number and generates an output binary number equal to the square of the input number.

a) Truth table →

Inputs		Outputs			
A	B	w	x	y	z
0	0	0	0	0	0
0	1	0	0	0	1
1	0	0	1	0	0
1	1	1	0	0	1

b) Minimised Boolean Expression →

For $w \rightarrow$

A \ B	0	1
0	0	0
1	0	1

$$w = AB$$

For $x \rightarrow$

A \ B	0	1
0	0	0
1	1	0

$$x = AB'$$

For $y \rightarrow$

A \ B	0	1
0	0	0
1	0	0


$$y = 0$$

For $z \rightarrow$

A \ B	0	1
0	0	1
1	0	1

$$z = B$$

c) Circuit Diagram →

 

d) HDL code →

```

library ieee;
use ieee.std_logic_1164.all;
entity test2 is
    port (A, B : in std_logic;
          W, X, Z : out std_logic);
end test2;
architecture boolean_eq of test2 is
    signal a : std_logic;
begin
    a <= NOT B;
    W <= A AND B;
    X <= A AND a;
    Z <= B;
end boolean_eq;
    
```

For Obj. 3 → Design, construct and test a circuit that generates an even parity bit from four message bits.

a) Truth table →

Input				Output
A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0


b) Minimized Boolean Circuit →

For F →

AB \ CD	00	01	11	10
00	0	1	0	1
01	1	0	1	0
11	0	1	0	1
10	1	0	1	0

$$\begin{aligned}
 F &= A'B'C'D + A'B'CD' + A'BC'D' + A'B'CD + ABC'D + ABC'D' \\
 &\quad + ABCD' + AB'C'D' + AB'CD \\
 &= A'B'(C'D + CD') + A'B(C'C'D + CD) + AB(C'D + CD') \\
 &\quad + AB'(C'D' + CD) \\
 &= (A'B' + AB)(C'D + CD') + (A'B + AB')(C'D' + CD) \\
 &= (A \oplus B)(C \oplus D) + (A \oplus B)(\overline{C \oplus D}) \\
 &= A \oplus B \oplus C \oplus D
 \end{aligned}$$

c) Circuit Design →

 

d) HDL code →

```
library ieee;  
use ieee.std_logic_1164.all;  
entity test3 is  
    port (A, B, C, D: in std_logic;  
          F: out std_logic);
```

```
end test3;
```

```
architecture boolean_eq of test3 is  
    signal a, b: std_logic;
```

```
begin
```

```
    a: A XOR B;
```

```
    b: a XOR C;
```

```
    F: b XOR D;
```


```
end boolean_eq;
```

IV) POST LAB →

Q1) What do you understand by the term majority logic?

Ans → Majority logic, a type of Boolean logic, is defined to be true if more than half of the n inputs are true, where n is odd.

 Q2) Suggest a suitable modification to be made in existing even parity circuit that can be used to generate bit for odd parity.



Q3) What is the function of a magnitude comparator circuit?

Ans → A digital comparator or magnitude comparator ~~circuit~~ is a hardware electronic device that takes two numbers as input in binary form & determines whether one number is greater than, less than or equal to the other numbers.

III) LAB →

Obj. 1 → It can be concluded for this combinational circuit we need 4 not gates, 4 ~~ex~~-or gates and 3 and gates.

Obj. 2 → It can be concluded for this combinational circuit we need 2 and gates and 1 not gate.

Obj. 3 → It can be concluded for this combinational circuit we need 3 ex-or gates to generate an even parity bit from 4 message bits.