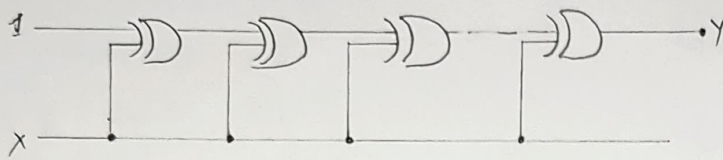


Q1) If the input to the digital circuit of the below figure consisting of a cascade of 4  $\text{XOR}$  gates is  $X$ , then what is the output  $Y$ ?




X	Y	0
0	0	0
0	1	1
1	0	1
1	1	0

Ans  $\rightarrow$  When one of the input to an XOR gate is 1, the output is simply the inverted value of the other input. Output of 1st XOR gate will be  $\rightarrow$

$$1 \oplus X = \bar{X}. \text{ Then, 2nd output } \rightarrow \bar{X} \oplus X = 1$$

Then  $\therefore$  For 4 such gates, the output of  $Y$  will be 1.

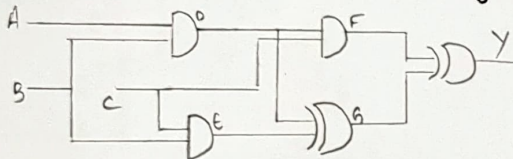Q2) The output of the combinational circuit given below is



Ans  $\rightarrow$   $D = AB, E = CB, F = DC, G = DE, Y = F \oplus G$

$$Y = F \oplus G$$

$$= DC \oplus (D \oplus E)$$

$$= ABC \oplus (ABC \oplus CB)$$


$$= ABC \oplus (ABC\bar{B} + \bar{A}BCB)$$

$$= ABC \oplus (ABC + \bar{A}BC)$$

$$= ABC(\bar{A}B + \bar{A}BC) + \bar{A}BC(\bar{A}B + \bar{A}BC)$$

$$= B(A + C)$$

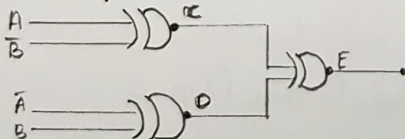Q3) The output of the circuit shown in Fig. is equal to



Ans  $\rightarrow$   $C = AB, D = \bar{A}\bar{B} + \bar{A}B + A\bar{B}, E = C \oplus D$   
 $= \bar{A}\bar{B} + \bar{A}B$

$$E = C \oplus D$$

$$= \bar{C}D + CD$$

$$= (\bar{A}\bar{B} + \bar{A}B)(\bar{A}\bar{B} + \bar{A}B) + (\bar{A}\bar{B} + \bar{A}B)(\bar{A}\bar{B} + \bar{A}B)$$

$$= 1$$

Q4) The number of product terms in the minimised sum-of-product expression obtained through the following k-map is (where, 'd' denotes don't care states)


Ans  $\rightarrow F(A, B, C, D) = B'D' + ACD'$

So, No. of product terms  $\rightarrow 2$

Q5) For the circuit shown in the following fig.,  $I_0 - I_3$  are inputs to the 4:1 multiplexer. R (maxB) and S are control bits  $\rightarrow$

Ans  $\rightarrow$  Truth Table

R	S	Z
0	0	$I_3 = P$
0	1	$I_2 = PCQ$
1	0	$I_1 = P$
1	1	$I_0 = P\bar{C}Q$

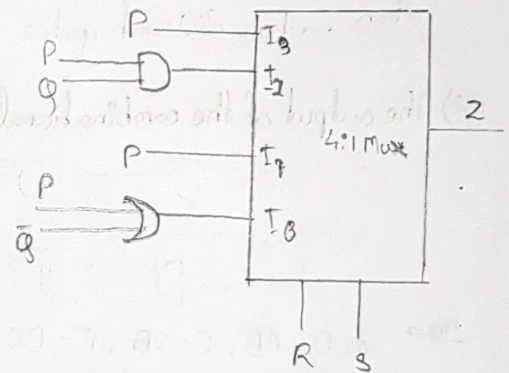

$$Z = P\bar{R}\bar{S} + PQR\bar{S} + PR\bar{S} + P\bar{C}QRS$$

Q6) The Boolean expression F implemented by the circuit is  $\rightarrow$


Ans  $\rightarrow M = X'Y + X \cdot 0 = X'Y$

$$F = Z'M + ZM'$$


$$= Z'X'Y + Z(X'Y)'$$

$$= Z'X'Y + Z(X+Y)'$$

$$= Z'X'Y + ZX + ZY$$

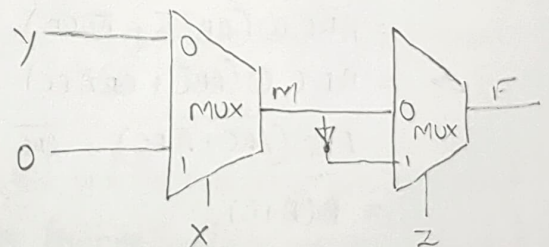

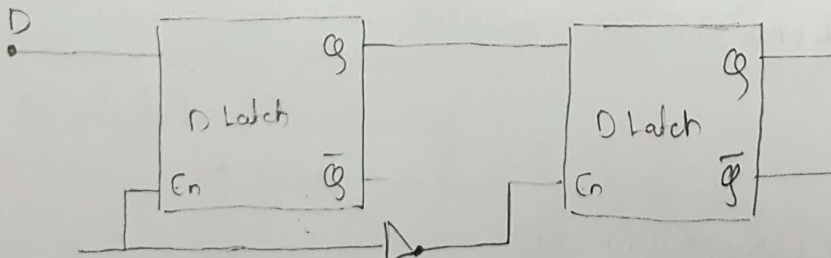Q7) The circuit shown in the fig. is a  $\rightarrow$  d) Master-Slave D Flip-flop



Q8) The initial contents of the 4-bit serial-in-parallel-out, right shift, shift register, shown in the fig. is 0110. After three clock pulses are applied, the contents of the Shift Register will be  $\rightarrow$



At pulse 1 input,  $1 \oplus 0 = 1$


So, contents are 1011

At pulse 2 input,  $1 \oplus 1 = 0$


Contents are 0101

At pulse 3 input,  $0 \oplus 1 = 1$

So, Contents are 1010.

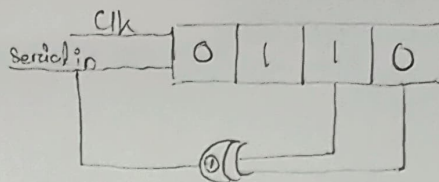

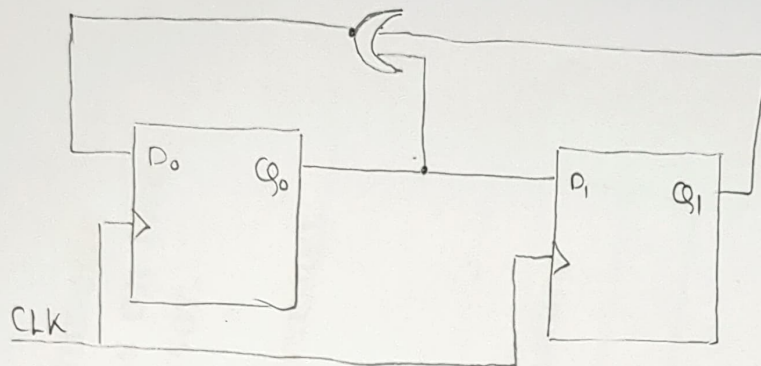Q9) For the circuit below, the counter state  $(Q_1, Q_0)$  follows the sequence



b) 00, 01, 10, 00, 01, ...

Q10) Briefly explain the following representations: sign magnitude, two's complement, biased.

Ans → Sign Magnitude → The leftmost bit is the sign bit, and the remaining bits represent the magnitude. A 0 represents a positive number, and a 1 represents a negative number.

Two's complement → The leftmost bit is the sign bit, and the remaining bits represent the two's complement of their absolute values. Positive numbers are represented the same way as in sign magnitude.

Biased → A fixed value, called the bias, is added to the integer. The leftmost bit forces the sign of the number, 0 with 0 representing positive & 1 representing negative.

Q12) Assume numbers are represented in 8-bit two's complement representation. Show the calculation of the following:

a)  $6 + 13$     b)  $-6 + 13$     c)  $6 - 13$     d)  $-6 - 13$

Ans → a)  $6 \rightarrow 00000110$   
 $13 \rightarrow 00001101$   
 $\quad \quad \quad +$   
 $\quad \quad \quad 00010011 (19)$

b)  $-6 \rightarrow 1111010$   
 $13 \rightarrow 00001101$   
 $\quad \quad \quad +$   
 $\quad \quad \quad 00000111 (7)$

c)  $6 \rightarrow 00000110$   
 $13 \rightarrow -00001101$   
 $\quad \quad \quad +$   
 $\quad \quad \quad 11110111 (-7)$

$$\begin{array}{r}
 d) -6 \rightarrow 11111010 \\
 -13 \rightarrow 00001101 \\
 \hline
 11101111 \quad (-19)
 \end{array}$$