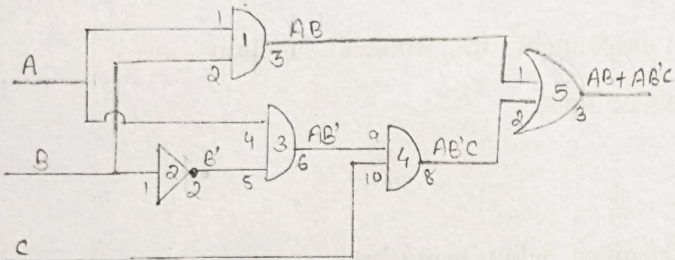


PRE-LAB

1) For Obj. 1 →

$$F(A, B, C) = AB + AB'C$$

a) Circuit Diagram →




b) Truth tables →

Inputs			Outputs			
A	B	C	B'	AB	AB'C	F = AB + AB'C
0	0	0	1	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	1	0	1	1
1	1	0	0	1	0	1
1	1	1	0	1	0	1

2) For Obj. 2 →

$$F(X, Y, Z) = XY + X'Z + YZ$$

a) Circuit Diagram →

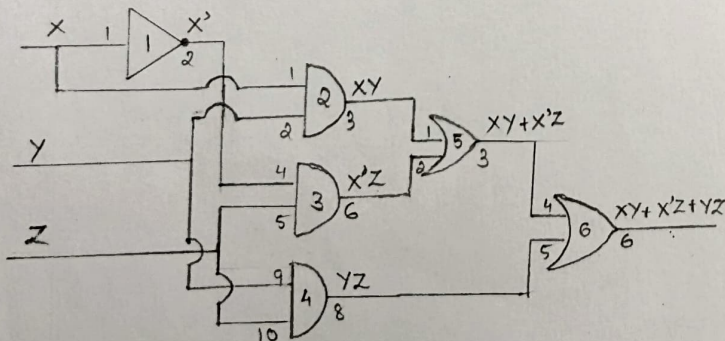


b) Truth Tables →

Inputs			Outputs				
X	Y	Z	X'	XY	X'Z	YZ	F = XY + X'Z + YZ
0	0	0	1	0	0	0	0
0	0	1	1	0	1	0	1
0	1	0	1	0	0	0	0
0	1	1	1	0	1	1	1
1	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0
1	1	0	0	1	0	0	1
1	1	1	0	1	0	1	1

3) For Obj. 3 →

$$F(X, Y, Z) = (X'Y' + Z)' + YZ$$

a) Circuit Diagram →

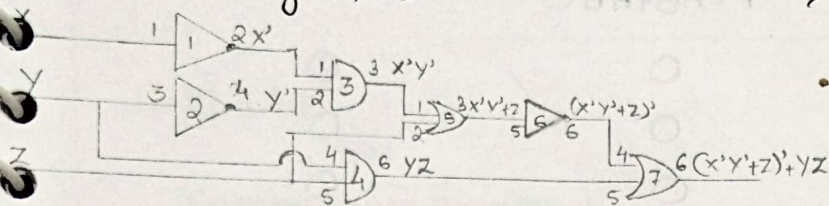

b) Truth tables →

Inputs			Outputs			
X	Y	Z	X'Y'	YZ	(X'Y' + Z)'	F = (X'Y' + Z)' + YZ
0	0	0	1	0	0	0
0	0	1	1	0	0	0
0	1	0	0	0	1	1
0	1	1	0	1	0	1
1	0	0	0	0	1	1
1	0	1	0	0	0	0
1	1	0	0	0	1	1
1	1	1	0	0	1	1

III) LAB:

Components Required →

Sl. No.	Name of the Component	Specification	Quantity
1	7404 IC	Hex Inverter	1
2	7408 IC	Quad 2 input AND gate	1
3	7432 IC	Quad 2 input OR gate	1
4	Universal Trainer Kit	—	1
5	Connecting Wires	23 SWG	As required

Observation →

$$F(X, Y, Z) = (X'Y' + Z)' + YZ$$

Inputs			Theoretical Output				Practical Output
X	Y	Z	X'Y'	YZ	(X'Y' + Z)'	F = (X'Y' + Z)' + YZ	
0	0	0	1	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	1	1	1
0	1	1	0	1	0	1	1
1	0	0	0	0	1	1	1
1	0	1	0	0	0	0	0
1	1	0	0	0	1	1	1
1	1	1	0	1	1	1	1

a) $F(A, B, C) = AB + AB'C$

Inputs			Theoretical Outputs				Practical Outputs
A	B	C	B'	AB	AB'C	$F = AB + AB'C$	
0	0	0	1	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	1	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	1	0	1	1	1
1	1	0	0	1	0	1	1
1	1	1	0	1	0	1	1

b) $F(X, Y, Z) = XY + X'Z + YZ$

Inputs			Theoretical Outputs				Practical Outputs
X	Y	Z	X'	XY	X'Z	YZ	$F = XY + X'Z + YZ$
0	0	0	1	0	0	0	0
0	0	1	1	0	1	0	1
0	1	0	1	0	0	0	0
0	1	1	1	0	1	1	1
1	0	0	0	0	0	0	0
1	0	1	0	0	1	0	1
1	1	0	0	1	0	0	1
1	1	1	0	1	0	1	1

III. LAB:

Components Required:

S. No	Name of the Component	Specification	Quantity
-------	-----------------------	---------------	----------

Observation:

Conclusion:

In this experiment implementing Boolean functions using logic gates. Some basics of logic gates (AND, OR, NOT) in sum of product representation of equation and their implementation using logic gates & also implementation of Boolean expression using Universal gates (NAND or NOR).

IV. POST LAB:

1. Prove the following equation using truth table:

$$(X+Y)(X'+Z) = XZ + X'Y$$

2. Draw a gate circuit which has an output $Z = [BC' + F(E+AD')]'$


3. Write truth table for the function $F = A(B+C') + 1$

Ans →

$$1) (X+Y)(X'+Z) = XZ + X'Y$$

Inputs			Outputs							
X	Y	Z	X'	XZ	X'Y	X+Y	X'Z	(X+Y)(X'+Z)		
0	0	0	1	0	0	0	1	0		0
0	0	1	1	0	0	0	1	0		0
0	1	0	1	0	1	1	1	1		1
0	1	1	1	0	1	1	1	1		1
1	0	0	0	0	0	1	0	0		0
1	0	1	0	1	0	1	1	1		1
1	1	0	0	0	1	1	0	0		1
1	1	1	0	1	1	1	1	1		1

$$2) Z = [BC' + F(E+AD')]'$$

 

$$3) F = A(B+C') + 1$$

Inputs			Outputs			
A	B	C	C'	B + C'	A(B+C')	F = A(B+C') + 1
0	0	0	1	1	0	1
0	0	1	0	0	0	1
0	1	0	1	1	0	1
0	1	1	0	1	0	1
1	0	0	1	1	0	1
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1