 



Q1) Construct a 16×1 multiplexer with two 8×1 and one 2×1 multiplexers. Use block diagrams.

Ans →



Q2) Construct a 5 to 32 line decoder with four 3 to 8 line decoders with enable and 2 to 4 line decoder. Use block diagrams for the components.

Ans →

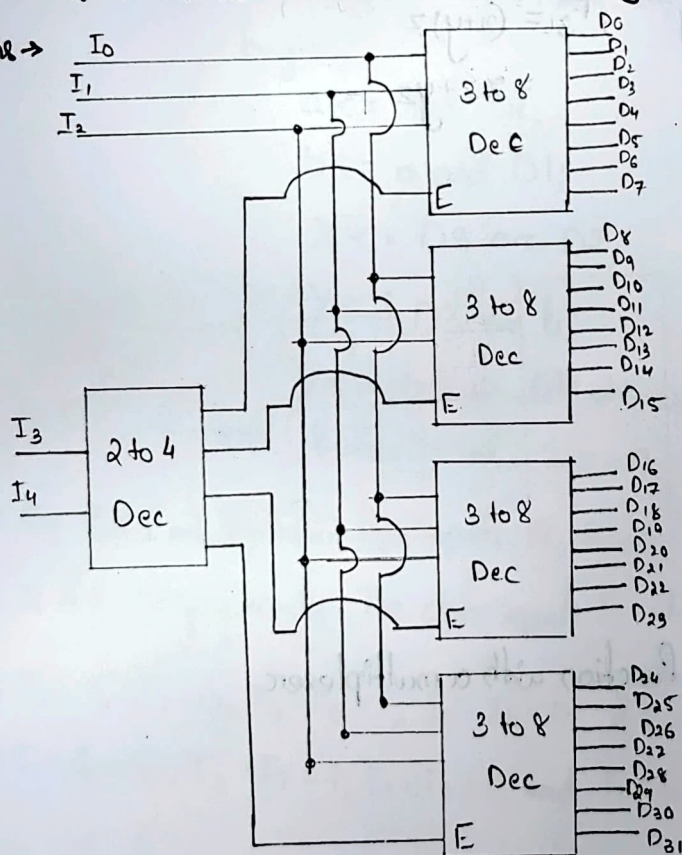

Q3) Using a decoder and external gates, design the combinational circuit defined by the following three Boolean functions:

a) $F_1 = x'y'z' + xz$, $F_2 = xy'z' + x'y$, $F_3 = x'y'z' + xy$


b) $F_1 = (y' + x)z$, $F_2 = y'z' + x'y + yz'$, $F_3 = (x + y)z$

Ans → a) $F_1 = x'y'z' + xz$, $F_2 = xy'z' + x'y$, $F_3 = x'y'z' + xy$

Truth table →

	X	Y	Z	F_1	F_2	F_3
D_0	0	0	0	0	0	1
D_1	0	0	1	0	0	0
D_2	0	1	0	1	1	0
D_3	0	1	1	0	1	0
D_4	1	0	0	0	1	0
D_5	1	0	1	1	0	0
D_6	1	1	0	0	0	1
D_7	1	1	1	1	0	1


Circuit →

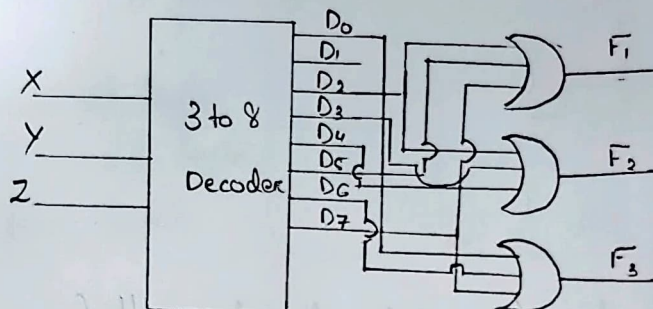

b) $F_1 = (y' + x)z$, $F_2 = y'z' + x'y + yz'$, $F_3 = (x + y)z$
 $= y'z + xz$ $= xz + yz$

Truth table →

	X	Y	Z	F_1	F_2	F_3
D_0	0	0	0	0	1	0
D_1	0	0	1	1	0	0
D_2	0	1	0	0	1	0
D_3	0	1	1	0	1	1
D_4	1	0	0	0	1	0
D_5	1	0	1	1	0	1
D_6	1	1	0	0	1	0
D_7	1	1	1	1	0	1

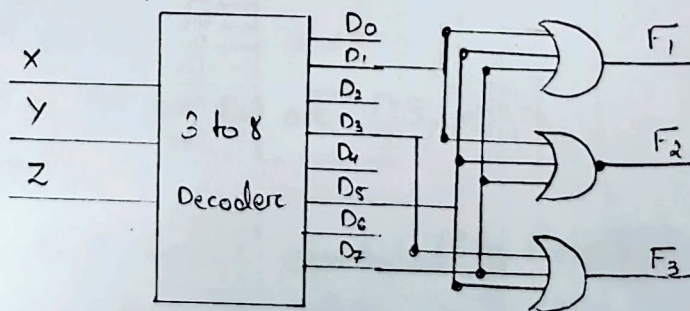


Q4) Implement the following Boolean function with a multiplexer

a) $F(A, B, C, D) = \Sigma(0, 2, 5, 8, 10, 14)$

b) $F(A, B, C, D) = \Pi(2, 6, 11)$


a) $F(A, B, C, D) = \sum (0, 2, 5, 8, 10, 14)$

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

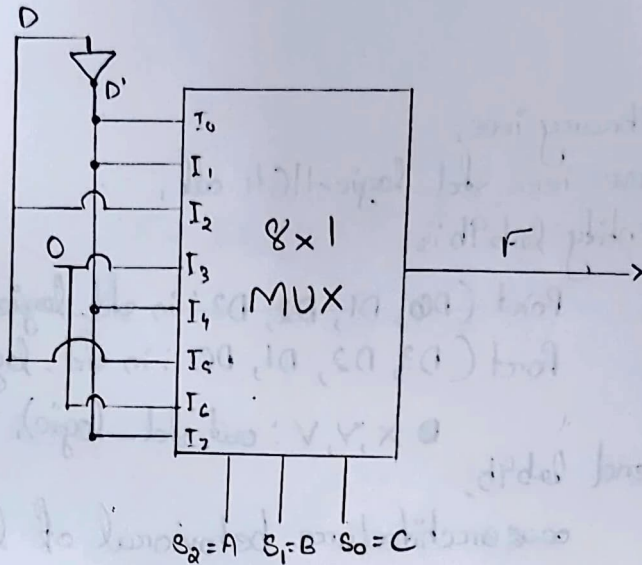


b) $F(A, B, C, D) = \prod (2, 6, 11)$

A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

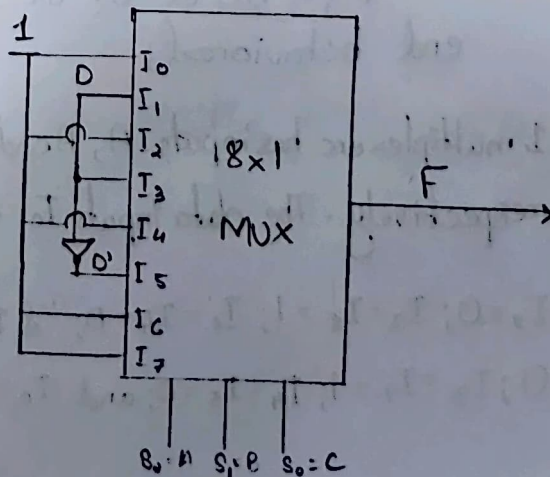

 Q5) Write the HDL description of 4 bit priority encoder circuit given below.



Ans →

```

library ieee;
use ieee.std_logic_164.all;
entity lab9b is
    Port (D0, D1, D2, D3 : in std_logic;
          D3, D2, D1, D0 : in std_logic;
          X, Y, V : out std_logic);
end lab9b;
-- architecture behavioral of lab9 is
    signal a, b : std_logic;
begin
    a <= not D2;
    b <= a and D1;
    X <= D3 or D2;
    Y <= D3 or b;
    V <= D0 or D1 or D2 or D3;
end behavioral;
  
```

Q6) An 8x1 multiplexer has inputs A, B and C connected to the selection inputs S_2, S_1 & S_0 respectively. The data inputs I_0 through I_7 are as follows -

a) $I_1 = I_2 = I_7 = 0$; $I_3 = I_5 = 1$; $I_0 = I_4 = D$; & $I_6 = D'$

b) $I_1 = I_2 = 0$; $I_3 = I_7 = 1$; $I_4 = I_5 = D$; and $I_0 = I_6 = D'$.

Ans → a) $I_1 = I_2 = I_7 = 0$; $I_3 = I_5 = 1$; $I_0 = I_4 = D$; $I_6 = D'$

A	B	C	D	F	
0	0	0	0	0	$I_0 = D$
0	0	0	1	1	
0	0	1	0	0	$I_1 = 0$
0	0	1	1	0	
0	1	0	0	0	$I_2 = 0$
0	1	0	1	0	
0	1	1	0	1	$I_3 = 1$
0	1	1	1	1	
1	0	0	0	0	$I_4 = D$
1	0	0	1	1	
1	0	1	0	1	$I_5 = 1$
1	0	1	1	1	
1	1	0	0	1	$I_6 = D'$
1	1	0	1	0	
1	1	1	0	0	$I_7 = 0$
1	1	1	1	0	

AB \ CD	00	01	11	10
00		1		
01			1	1
11	1			
10		1	1	1

$$F = ABC'D' + B'C'D + A'BC + AB'C$$


b) $I_1 = I_2 = 0$; $I_3 = I_7 = 1$; $I_4 = I_5 = D$; and $I_0 = I_6 = D'$

A	B	C	D	F	
0	0	0	0	1	$I_0 = D'$
0	0	0	1	0	
0	0	1	0	0	$I_1 = 0$
0	0	1	1	0	
0	1	0	0	0	$I_2 = 0$
0	1	0	1	0	
0	1	1	0	1	$I_3 = 1$
0	1	1	1	1	
1	0	0	0	0	$I_4 = D$
1	0	0	1	0	
1	0	1	0	1	$I_5 = D$
1	0	1	1	1	
1	1	0	0	1	$I_6 = D'$
1	1	0	1	0	
1	1	1	0	1	$I_7 = 1$
1	1	1	1	1	

AB \ CD	00	01	11	10
00	1			
01			1	1
11	1		1	1
10		1	1	

$$F = A'B'C'D' + ABD' + AB'D + BC$$

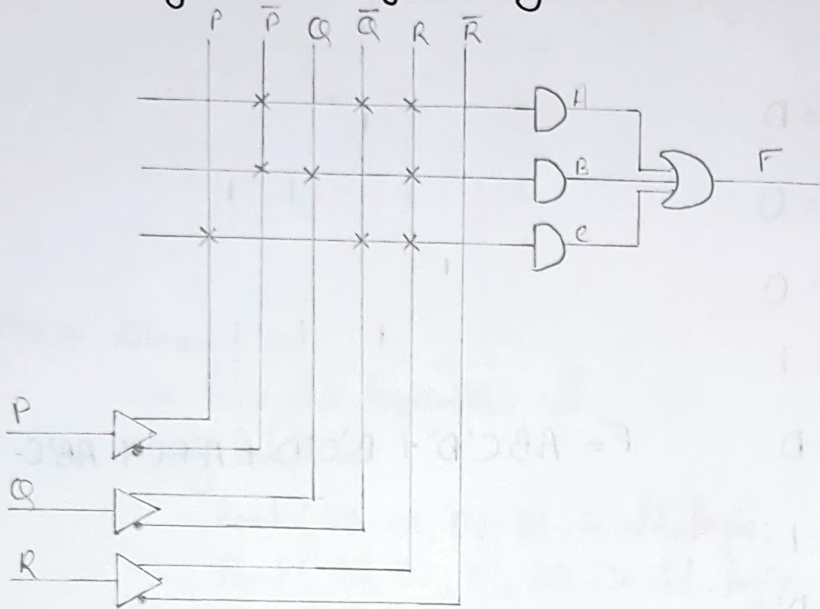Q7) A programmable logic array (PLA) is shown in the figure



Ans → From the above fig.,

$$A = \bar{P}\bar{Q}R, B = \bar{P}Q, R, C = P\bar{Q}R$$

$$F = A + B + C$$


$$= \bar{P}\bar{Q}R + \bar{P}Q, R + P\bar{Q}R$$

Q8) Draw a PLA circuit to implement the functions

$$F_1 = A'B + AC + A'BC'$$

$$F_2 = (AC + AB + BC)'$$

Ans →

 

Q79) Implement full adder using PAL.

Ans →

A	B	C _{in}	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

A \ BC _{in}	00	01	11	10
0		1		1
1	1		1	

$$S = A'B'C_{in} + A'BC_{in}' + AB'C_{in}' + ABC_{in}$$

A \ BC _{in}	00	01	11	10
0			1	
1		1	1	1

$$C = BC_{in} + AC_{in} + AB$$

