

I) PRE-LAB →

For Obj. 1 → Design a 2 bit Comparator circuit.

a) Truth table →

Input				Output		
A ₁	A ₀	B ₁	B ₀	A > B	A < B	A = B
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	0	1

b) Minimised Boolean expression →

i) For A > B →

ii) For A < B →

iii) For A = B →

A ₁ B ₁ B ₀	00	01	11	10
00	0	0	0	0
01	1	0	0	0
11	1	1	0	1
10	1	1	0	0

A ₁ A ₀ B ₁ B ₀	00	01	11	10
00	0	1	1	1
01	0	0	1	1
11	0	0	0	0
10	0	0	1	0

A ₁ A ₀ B ₁ B ₀	00	01	11	10
00	1	0	0	0
01	0	1	0	0
11	0	0	1	0
10	0	0	0	1

$$A > B = A_1 B_1' + A_0 B_1' B_0' + A_1 A_0 B_0'$$

$$A < B = A_1' B_1 + A_1' B_1 B_0 + A_1' A_0' B_0$$

$$(A = B) = (A_0 \oplus B_0) (A_1 \oplus B_1)$$

For A = B →


$$F = A_1' A_0' B_1' B_0' + A_1' A_0 B_1' B_0 + A_1 A_0 B_1 B_0 + A_1 A_0' B_1 B_0'$$

$$= A_0' B_0' (A_1' B_1' + A_1 B_1) + A_0 B_0 (A_1' B_1' + A_1 B_1)$$

$$= (A_0 B_0 + A_0' B_0') (A_1' B_1' + A_1 B_1)$$

$$= (A_0 \odot B_0) (A_1 \odot B_1)$$

c) Circuit Diagram →

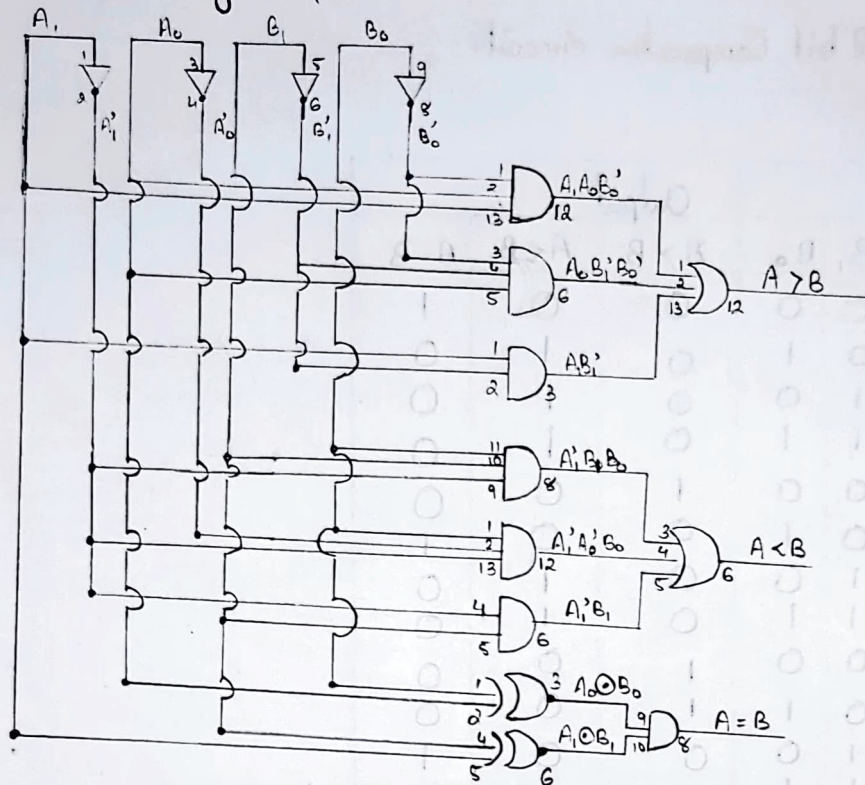

d) HDL code →

```
library ieee;
use ieee.std_logic_1164.all;
entity test1 is
    port CA1, AD, B1, BD : in std_logic;
```

```
    F1, F2, F3 : out std_logic;
end test1;
```

architecture boolean_eq of test1 is

signal A, B, C, D : std_logic;

signal a, b, c, d, e, f, g, h : std_logic;

A <= NOT A1;

B <= NOT B0;

C <= NOT B1;

D <= NOT B0;

a <= A1 AND A0 AND D;

b <= A0 AND C AND D;

c <= A1 AND C;

d <= A AND B1 AND BD;

e <= A AND B AND B0;

f <= A AND B1;

g <= A0 EX-NOR B0;

h <= A1 EX-NOR B0;

F1 = a OR b OR c;

F2 = d OR e OR f;

F3 = g AND h

end boolean_eq;

For Obj. 2 → Combinational circuit that converts 4 bit binary number to equivalent Gray code.

a) Truth Table →

Inputs				Outputs			
A	B	C	D	G ₃	G ₂	G ₁	G ₀
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	1	0	0
0	0	1	1	0	1	1	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	1
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	0
1	0	0	1	1	0	1	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	1	0
1	1	0	0	1	1	0	1
1	1	0	1	1	1	1	1
1	1	1	0	0	0	0	1
1	1	1	1	0	0	1	1

b) Minimised Boolean Expression →

i) For G₃ →

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	1	1	1
10	1	1	1	1

$$G_3 = A$$

ii) For G₂ →

AB \ CD	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

$$G_2 = A'B + AB' \\ = A \oplus B$$

iii) For G₁ →

AB \ CD	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	1	1	0	0
10	0	0	1	1


$$G_1 = B'C' + B'C \\ = B \oplus C$$

iv) For G₀ →

AB \ CD	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$G_0 = C'D + C'D \\ = C \oplus D$$

c) Circuit Diagram →

 

d) HDL code →

```

library ieee;
use ieee.std_logic_1164.all;
entity test2 is
    port (A, B, C, D : in std_logic;
          G3, G2, G1, G0 : out std_logic);
end test2;
architecture truth boolean_eq of test2 is
begin
    G3 <= A;
    G2 <= A XOR B;
    G1 <= B XOR C;
    G0 <= C XOR D;
end boolean_eq;

```

For Obj. 3 → Design a combinational circuit with four input lines that represents a decimal digit in BCD and four output lines that generates the 9's complement of the input digit.

a) Truth table →

Inputs				Outputs			
A	B	C	D	w	x	y	z
0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	0
0	0	1	0	0	1	1	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	0	0
0	1	1	0	0	0	1	1
0	1	1	1	0	0	1	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0

b) Minimized Boolean Expression →

For w →

AB \ CD	00	01	11	10
00	1	1	0	0
01	0	0	0	0
11	x	x	x	x
10	0	0	x	x

$$w = A'B'C'$$

For x →

AB \ CD	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	x	x	x	x
10	0	0	x	x

$$x = BC' + B'C = B \oplus C$$

For y →

AB \ CD	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	x	x	x	x
10	0	0	x	x


$$y = C$$

For z →

AB \ CD	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	x	x	x	x
10	1	0	x	x

$$z = D'$$

c) Circuit Diagram →

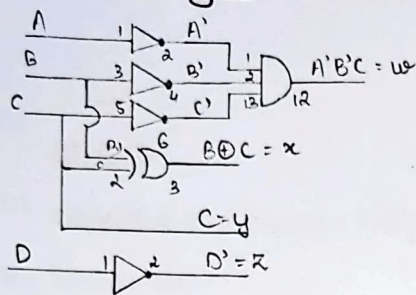

d) HDL code →

```


library ieee;
use ieee.std_logic.1164.all;
entity test3 is
    port CA, B, C, D : in std_logic;
          W, X, Y, Z : out std_logic;
end test3;
architecture boolean_eq of test3 is
    signal a, b, c : std_logic;
begin
    a <= NOT A;
    b <= NOT B;
    c <= NOT C;
    W <= a AND b AND c;
    X <= B XOR C;
    Y <= C;
    Z <= NOT D;
end boolean_eq;
    
```


IV > POST LAB →


1) Design a 3 bit majority circuit.

Ans →

Inputs			Output
A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

$$F = AB + BC + AC$$

 


2) What is the advantage of Gray code?

Ans → The advantage of Gray code is that just one bit changes for each step. This will come in handy in circuits that are sensitive to glitches and other errors.

3) Draw the logic circuit that converts 4 bit Gray code to binary code.

Ans →

 

III > LAB →

Conclusion →

Obj 1 → It can be concluded that for a 2 bit Comparator circuit we need 3 7 and gates, 2 or gates and 2 ex-nor gates to get $A < B$, $A > B$ & $A = B$.

Obj 2 → It can be concluded that for to convert a 4-bit binary to equivalent gray code we need 3 ex-or gates.

Obj 3 → It can be concluded that for a 9's complement of a BCD number we need 4 not gates, 1 ex-or gate and 1 and gate.