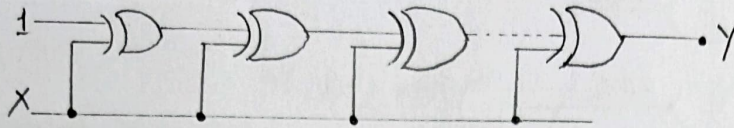


Q1) If the input to the digital circuit of the below figure consisting of a cascade of 20 XOR gates is X, then what is the output Y?



Ans → The truth table for an XOR Gate →

When one of the input to an XOR gate is 1, the output is simply the inverted value of the other input.


Output of 1st XOR gate will be  $\rightarrow 1 \oplus X = \bar{X}$

Then, 2nd output  $\rightarrow \bar{X} \oplus X = 1$

∴ For 20 such gates, the output of Y will be 1.

X	Y	O
0	0	0
0	1	1
1	0	1
1	1	0

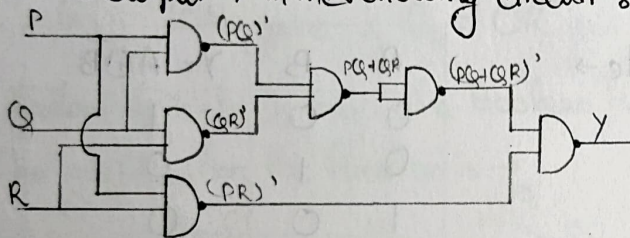
Q2) The output Y in the following circuit shown below is always 1 when



Ans → Hence, the output  $Y = PQ + QR + PR$  as we can see from above diagram

If 2 or more inputs are 1, then only it will be 1.

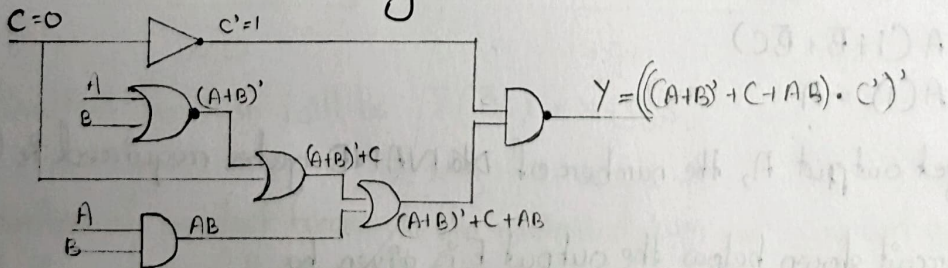Q3) In the circuit shown in the fig., if  $C = 0$ , the expression for Y is



Ans → From the above fig,  $Y = ((A+B)' + C + AB) \cdot C'$

$$= ((A+B)' + AB) \quad (\text{As } C = 0 \text{ \& } C' = 1)$$


$$= (\bar{A}\bar{B} + AB)$$

$$= \bar{A} \odot B$$

$$= A \oplus B$$



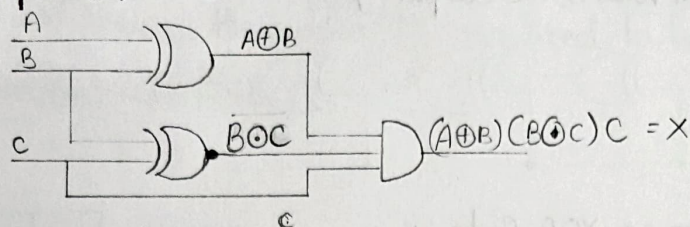Q4) For the logic circuit shown in the fig., the required input condition (A,B,C) to make the output (X)=1 is




Ans → For,  $X=1$ ,

$$A \oplus B = 1, \text{ i.e. } A=0, B=1$$

$$B \oplus C = 1; \text{ i.e. } B=1, C=1$$

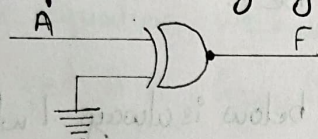Q5) The output of the logic gate in fig. is



Ans → Truth table for XNOR gate →

$$\text{Output equation} \Rightarrow Y = \overline{A \oplus B}$$

$$\text{As B is low, } Y = \overline{A \oplus 0} = \overline{A}$$

A	B	$Y = \overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

Q6) The minimum number of NAND gates required to implement the Boolean function  $A + A\bar{B} + A\bar{B}C$  is equal to \_\_\_\_.


Ans →  $F = A + A\bar{B} + A\bar{B}C$

$$= A(1 + \bar{B} + \bar{B}C)$$

$$= A(1) = A$$

∴ To get output A, the number of NAND gates required is 0.

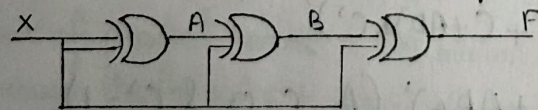Q7) For the circuit shown below the output F is given by



Ans →  $A = X \oplus X = 0$


$$B = A \oplus X = 0 \oplus X = X$$

$$F = X \oplus X = 0$$

$$\therefore F = 0$$



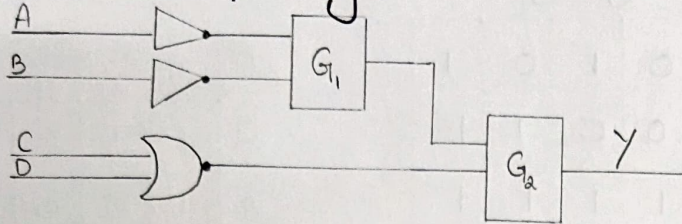Q) In the figure shown, the output  $Y$  is required to be  $Y = A \cdot B + \bar{C} \cdot \bar{D}$ . The gates  $G_1$  &  $G_2$  must be respectively:



Ans → The NOR gate takes the input  $C$  &  $D$  will give the output as  $\overline{A \cdot C + D}$  or  $\bar{C} \cdot \bar{D}$ .

$$\therefore F = A \cdot B + \bar{C} \cdot \bar{D}$$

From the equation, we have  $\bar{C} \cdot \bar{D}$ , So, the  $G_2$  will be OR gate.

Next to get  $A \cdot B$ , from the fig.  $\bar{A}$  &  $\bar{B}$  has to pass through the NOR gate.

$\therefore G_1 = \text{NOR gate}$  &  $G_2 = \text{OR gate}$ .

Q) Following is the k-map of a Boolean function of five variables  $P, Q, R, S$  &  $X$ .

The minimum for the function is →

RS \ PQ	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	0	0	1
10	0	0	0	0

$X=0$

RS \ PQ	00	01	11	10
00	0	1	1	0
01	0	0	0	0
11	0	0	0	0
10	0	1	1	0

$X=1$

Ans → Resultant function will be  $\bar{X}(\bar{Q}S) + X(Q\bar{S})$

$$= x'q's + x'q's'$$

10) The number of product terms in the minimised sum-of-product expression obtained through the following k-map is (where 'd' denotes don't care states).

1	0	0	1
0	d	0	0
0	0	d	1
1			1

Ans → So, from the fig., we get that there will be 2 SOP.




11) The truth table for the output  $Y$  in terms of three inputs  $A, B$  &  $C$  are given in Table. Draw a logic circuit realization using only NOR gates.

	0	1	2	3	4	5	6	7
A	0	1	0	1	0	1	0	1
B	0	0	1	1	0	0	1	1
C	0	0	0	0	1	1	1	1
Y	1	1	1	0	1	0	0	0


BA \ C	00	01	11	10
0	1	1	0	1
1	1	0	0	0

Ans → From the k-map, we get  $Y_{POS} = (C+B)(A+B)(A+C)$

$$Y_{SOP} = (A'B') + (A'C') + (B'C')$$

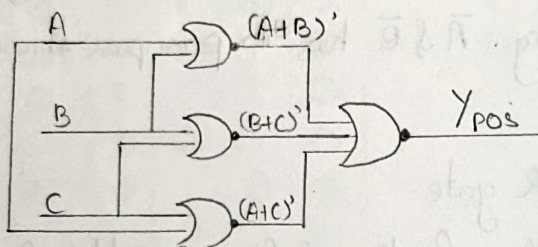

12)

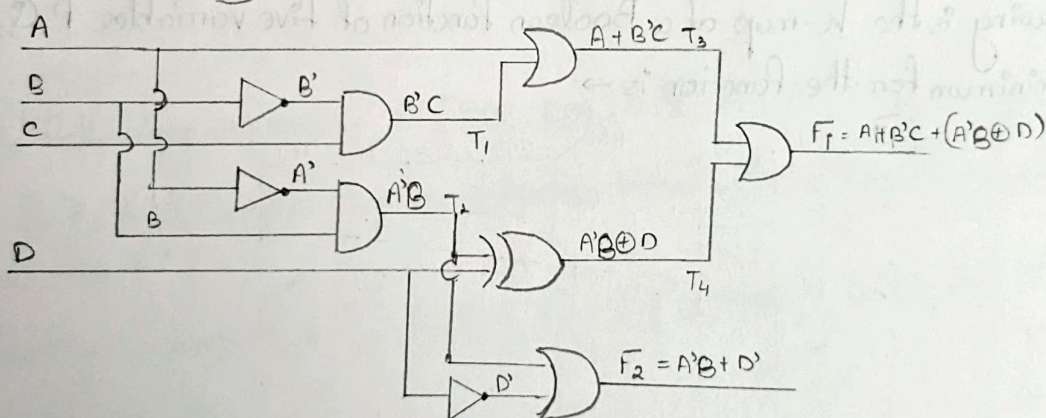

Consider the combinational circuit shown above →

a) Derive the Boolean expressions for  $T_1$  through  $T_4$ . Evaluate the outputs  $F_1$  &  $F_2$  as a function of 4 inputs.

b) List the truth table with 16 binary combinations of the four input variables. Then list the binary values for  $T_1$  through  $T_4$  and outputs  $F_1$  &  $F_2$  in the table.

Ans → a)  $T_1 = B'C$ ,  $T_2 = A'B$ ,  $T_3 = A + B'C$ ,  $T_4 = A'B \oplus D = A'B'D' + A'B'D$

$$\begin{aligned} F_1 &= T_3 + T_4 = A + B'C + A'B'D' + A'B'D + AD \\ &= A(1+D) + A'B'D' + B'C + B'D \\ &= (A+A')(A+BD') + B'C + B'D \\ &= A + BD' + B'C + B'D \end{aligned}$$

$$\begin{aligned} &= A'B'D' + (A+B')D \\ &= A'B'D' + AD + B'D \end{aligned}$$



$$F_2 = A'B + D'$$

b) Truth Table  $\rightarrow$

Inputs				Outputs					
A	B	C	D	T <sub>1</sub>	T <sub>2</sub>	T <sub>3</sub>	T <sub>4</sub>	F <sub>1</sub>	F <sub>2</sub>
0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	1	1	0
0	0	1	0	1	0	1	0	1	1
0	0	1	1	1	0	1	1	1	0
0	1	0	0	0	1	0	1	1	1
0	1	0	1	0	1	0	0	0	1
0	1	1	0	0	1	0	1	1	1
0	1	1	1	0	1	0	0	1	1
1	0	0	0	0	0	1	0	0	1
1	0	0	1	0	0	1	1	1	0
1	0	1	0	1	0	1	0	1	1
1	0	1	1	1	0	1	1	1	0
1	1	0	0	0	0	1	0	1	1
1	1	0	1	0	0	1	1	1	0
1	1	1	0	0	0	1	0	1	1
1	1	1	1	0	0	1	1	1	0

13) Consider the following expression  $F(P, Q, R, S) = \sum(0, 2, 5, 7, 8, 10, 13, 15)$ .

The minterms 0, 7, 8 & 13 are don't-care terms. What is the minimal sum-of-products form for F?

Ans  $\rightarrow$  Plotting k-map for  $F(P, Q, R, S) = \sum(0, 2, 5, 7, 8, 10, 13, 15)$

RS \ PQ	00	01	11	10
00	1			X
01		1	X	
11		X	1	
10	X			1

From the k-map,

$$\begin{aligned}
 F_{\text{sop}} &= QS + \overline{Q}\overline{S} \\
 &= Q \oplus S \\
 &= \overline{Q \oplus S}
 \end{aligned}$$



14) Let the minterm expression  $F(A, B, C, D) = \sum_m(0, 2, 4, 6, 8) + \sum_d(1, 3, 10)$ . What is the minimal form of the function represented by the Karnaugh map?

Ans → Plotting the k-map for  $F(A, B, C, D) = \sum_m(0, 2, 4, 6, 8) + \sum_d(1, 3, 10)$

AB \ CD	00	01	11	10
00	1	X	X	1
01	1			1
11				X
10	1			X

From the k-map,

$$F_{\text{sop}} = B'D' + A'D'$$

$$= A'D'(B' + B) = A'D'$$

15) What is the minimum SOP for  $F(w, x, y, z) = \sum_m(4, 6, 9, 11, 12, 14) + \sum_d(1, 3, 10)$ ?

Ans → Plotting the k-map for  $F(w, x, y, z) = \sum_m(4, 6, 9, 11, 12, 14) + \sum_d(1, 3, 10)$

wx \ yz	00	01	11	10
00		X	X	
01	1			1
11	1			1
10		1	1	X

From the k-map,

$$F_{\text{sop}} = xz' + x'z$$

$$= x \oplus z$$

16) Implement the 4-variable function using minimum number of 2-input NOR gates, which is expressed in sum-of-minterms form as  $F = \sum(0, 2, 5, 7, 8, 10, 13, 15)$ .

Ans → Plotting the k-map for  $F(A, B, C, D) = \sum(0, 2, 5, 7, 8, 10, 13, 15)$

AB \ CD	00	01	11	10
00	1			1
01		1	1	
11		1	1	
10	1			1


From the k-map,

$$F_{\text{sop}} = BD + B'D'$$

$$= \overline{B \oplus D}$$

$$= (B'D + BD')$$

$$= (B + D')(B' + D)$$

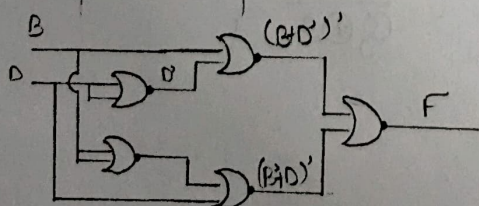



17) What is the minimum POS for  $F(A, B, C, D) = \sum m(1, 3, 4, 6, 9, 11, 12, 14)$ ?

Ans → Plotting the k-map for  $F(A, B, C, D) = \sum m(1, 3, 4, 6, 9, 11, 12, 14)$

AB \ CD	00	01	11	10
00		1	1	
01	1			1
11	1			1
10		1	1	

$$F_{\text{sop}} = B'D + BD'$$

$$\begin{aligned} \text{For } F_{\text{pos}} &= (F_{\text{sop}})' \\ &= (B'D + BD')' \\ &= (B + D')(B' + D) \\ &= (B + D)(B' + D') \end{aligned}$$

18) Consider the minterms list form of a Boolean function  $F(P, Q, R, S) = \sum m(0, 2, 5, 7, 9, 11) + \sum d(3, 8, 10, 12, 14)$ . Here, m denote a minterm & d denotes a don't care term, then what are the essential prime implicants of the function F?

Ans → Plotting the k-map for  $F(P, Q, R, S) = \sum m(0, 2, 5, 7, 9, 11) + \sum d(3, 8, 10, 12, 14)$

PQ \ RS	00	01	11	10
00	1		X	1
01		1	1	
11	X			X
10	X	1	X	1

From the k-map,

$$F_{\text{sop}} = P'QS + PQ' + Q'S'$$

∴ There are <sup>essential</sup> 3 prime implicants.