

Q1) The output Y of a 2-bit comparator is logic 1 whenever the 2-bit input A is greater than the 2-bit input B. The number of combinations for which the output is logic 1, is ____.

Ans → The only possible combinations are

$$A=01 \text{ \& } B=00$$

$$A=10 \text{ \& } B=00, 01$$

$$A=11 \text{ \& } B=00, 01, 10$$

So, there are 6 combinations

Q2) Find all prime implicants of the following function and then find all minimum solutions using petrick's method →

$$F(A, B, C, D) = \sum m(9, 12, 13, 15) + \sum d(1, 4, 5, 7, 8, 11, 14)$$

Ans →	Column 1	Column 2	Column 3
1	0001	1,5 0-01	1,5,9,13 --01 C'D
4	0100	1,9 -001	1,9,5,13 --01 C'D
8	1000	4,5 010-	4,5,12,13 -10- BC'
5	0101	4,12 -100	4,12,5,13 -10- BC'
9	1001	8,9 100-	5,7,13,15 -1-1 BD
12	1100	8,12 1-00	5,7,13,15 -1-1 BD
7	0111	5,7 01-1	8,9,12,13 1-0- AC'
11	1011	5,13 -101	8,12,9,13 1-0- AC'
13	1101	9,11 10-1	9,11,13,15 1--1 AD
14	1110	9,13 1-01	9,13,11,15 1--1 AD
15	1111	12,13 110-	12,13,14,15 11-- AB
		12,14 11-0	12,14,13,15 11-- AB
		7,15 -111	
		11,15 1-11	
		13,15 11-1	
		14,15 111-	

Prime implicants → C'D, BC', BD, AC', AD, AB

Petrick's table →

		9	12	13	15
P ₁ (1,5,9,13)	C'D	x		x	
P ₂ (4,5,12,13)	BC'		x	x	
P ₃ (5,7,13,15)	BD			x	x
P ₄ (8,9,12,13)	AC'	x	x	x	
P ₅ (9,11,13,15)	AD	x		x	x
P ₆ (12,13,14,15)	AB		x	x	x

By using Petrick's method,

$$\begin{aligned}
 P &= (P_1 + P_3 + P_5)(P_2 + P_3 + P_6)(P_1 + P_2 + P_3 + P_4 + P_5 + P_6)(P_4 + P_5 + P_6) \\
 &= (P_3 + (P_1 + P_5)(P_2 + P_6))(P_4 + P_5 + P_6(P_1 + P_2 + P_3 + P_6)) \\
 &= (P_3 + P_1P_2 + P_1P_6 + P_5P_2 + P_5P_6)(P_4 + P_5 + P_1P_6 + P_2P_6 + P_3P_6 + P_6) \\
 &= (P_3 + P_1P_2 + P_1P_6 + P_5P_2 + P_5P_6)(P_4 + P_5 + P_6(P_1 + P_2 + P_3 + 1)) \\
 &= (P_3 + P_1P_2 + P_1P_6 + P_2P_5 + P_5P_6)(P_4 + P_5 + P_6) \\
 &= \underline{P_3P_4} + P_1P_2P_4 + P_1P_6P_4 + P_2P_5P_4 + P_4P_5P_6 + \underline{P_3P_5} + P_1P_2P_5 + P_1P_6P_5 + \underline{P_2P_5} + \underline{P_5P_6} \\
 &\quad + \underline{P_3P_6} + P_1P_2P_6 + P_2P_5P_6 + P_5P_6 + \underline{P_1P_6}
 \end{aligned}$$

Simplified SOP $\rightarrow F_1 = P_3P_4 = AC' + BD$

$F_2 = P_3P_5 = AC' + AD$

$F_3 = P_2P_5 = BC' + AD$

$F_4 = P_5P_6 = AD + AB$

$F_5 = P_3P_6 = AC' + AB$

$F_6 = P_1P_6 = C'D + AD$

4) Determine a minimum sum of products expression for the function $F = \sum_m(0, 1, 2, 5, 6, 7)$ using Quine-McCluskey method and prime implicant chart.

Ans $\rightarrow F = \sum_m(0, 1, 2, 5, 6, 7)$

Column 1	Column 2	Prime implicants
0 \rightarrow 000	0, 1 \rightarrow 00-	$a'b'$
1 \rightarrow 001	0, 2 \rightarrow 0-0	$a'c'$
2 \rightarrow 010	1, 5 \rightarrow -01	$b'c$
5 \rightarrow 101	2, 6 \rightarrow -10	bc'
6 \rightarrow 110	5, 7 \rightarrow 1-1	ac
7 \rightarrow 111	6, 7 \rightarrow 11-	ab

Prime implicant chart →

	0	1	2	5	6	7
(0,1) $a'b'$	*	*				
(0,2) $a'c'$	*		*			
(1,5) $b'c$		*	*	*		
(2,6) bc'			*		*	
(5,7) ac				*	*	*
(6,7) ab					*	*

For the 1st solution,
 $F = a'b' + bc' + ac$

For the 2nd solution,
 $F = a'c' + b'c + ab$

Q3) Determine a minimum sum of products expression for the function $F = \sum m(0,1,2,5,6,7)$ using Petrick's method.

Ans → For Petrick's method we can directly use Q.4's prime implicant chart

	0	1	2	5	6	7
$P_1 - (0,1) a'b'$	x	x				
$P_2 - (0,2) a'c'$	x		x			
$P_3 - (1,5) b'c$		x		x		
$P_4 - (2,6) bc'$			x		x	
$P_5 - (5,7) ac$				x		x
$P_6 - (6,7) ab$					x	x

$$\begin{aligned}
 P &= (P_1 + P_2)(P_1 + P_3)(P_2 + P_4)(P_3 + P_5)(P_4 + P_6)(P_5 + P_6) \\
 &= (P_1 + P_2 P_3)(P_4 + P_2 P_6)(P_5 + P_3 P_6) \\
 &= (P_1 P_4 + P_2 P_3 P_4 + P_1 P_2 P_6 + P_2 P_3 P_6)(P_5 + P_3 P_6) \\
 &= \underline{P_1 P_4 P_5} + P_2 P_3 P_4 P_5 + P_1 P_2 P_5 P_6 + P_2 P_3 P_5 P_6 + P_1 P_3 P_4 P_6 + P_2 P_3 P_4 P_6 + P_1 P_2 P_3 P_6 \\
 &\quad + \underline{P_2 P_3 P_6}
 \end{aligned}$$

So, minimum SOP expression of the function,

for $P_1 P_4 P_5 = F = a'b' + bc' + ac$

for $P_2 P_3 P_6 = F = a'c' + b'c + ab$

Q) 5) Determine the a minimum sum of products expression for the function
 $F = \sum_m (1, 3, 4, 5, 6, 7, 10, 12, 13) + \sum_d (2, 9, 15)$ using Quine-McCluskey method
 and prime implicant chart.

Ans $\rightarrow F = \sum_m (1, 3, 4, 5, 6, 7, 10, 12, 13) + \sum_d (2, 9, 15)$

Column - 1	Column 2	Column - 3	Prime Implicants
1 \rightarrow 0001	1, 3 \rightarrow 00-1	1, 3, 5, 7 \rightarrow 0--1	$A'D$
2 \rightarrow 0010	1, 5 \rightarrow 0-01	1, 5, 3, 7 \rightarrow 0--1	
4 \rightarrow 0100	1, 9 \rightarrow -001	1, 5, 9, 13 \rightarrow --01	$C'D$
3 \rightarrow 0011	2, 3 \rightarrow 001-	1, 9, 5, 13 \rightarrow --01	
5 \rightarrow 0101	2, 6 \rightarrow 0-10	2, 3, 6, 7 \rightarrow 0-1-	$A'C$
6 \rightarrow 0110	2, 10 \rightarrow -010	2, 6, 3, 7 \rightarrow 0-1-	
9 \rightarrow 1001	4, 5 \rightarrow 010-	4, 5, 6, 7 \rightarrow 01--	$A'B$
10 \rightarrow 1010	4, 6 \rightarrow 01-0	4, 6, 5, 7 \rightarrow 01--	
12 \rightarrow 1100	4, 12 \rightarrow -100	4, 12, 5, 13 \rightarrow -10-	BC'
7 \rightarrow 0111	3, 7 \rightarrow 0-11	5, 13, 7, 15 \rightarrow -1-1	BD
13 \rightarrow 1101	5, 7 \rightarrow 01-1	5, 7, 13, 15 \rightarrow -1-1	
15 \rightarrow 1111	6, 7 \rightarrow 011-	2, 10 \rightarrow -010	$B'CD'$
	5, 13 \rightarrow -101	4, 5, 12, 13 \rightarrow -10-	
	9, 13 \rightarrow 1-01		
	12, 13 \rightarrow 110-		
	7, 15 \rightarrow -111		
	13, 15 \rightarrow 11-1		

Prime implicant chart \rightarrow

	1	3	4	5	6	7	10	12	13
(1, 3, 5, 7) $A'D$	*	*		*		*			
(1, 5, 9, 13) $C'D$	*			*					*
(2, 3, 6, 7) $A'C$		*			*	*			
(4, 5, 6, 7) $A'B$			*	*	*	*			
(4, 12, 5, 13) BC'			*	*				*	*
(5, 13, 7, 15) BD				*		*		*	*
(2, 10) $B'CD'$					*	*	*		

2 possible solⁿ are $\rightarrow F = BC' + B'CD' + C'D + A'C$

$$F = BC' + B'CD' + A'B + A'D$$

Q6) Using the method of map-entered variables, use four-variable maps to find a minimum sum-of-products expression for $F(A, B, C, D, E) = \sum_m(0, 4, 6, 13, 14) + \sum_d(2, 9) + E(m_1 + m_2)$.

Ans $\rightarrow F(A, B, C, D, E) = \sum_m(0, 4, 6, 13, 14) + \sum_d(2, 9) + E(m_1 + m_2)$

AB \ CD	00	01	11	10
00	1			X
01	1			1
11		1		1
10		X		

For $E=0$

$$MS_0 = A'D + BCD' + AC'D$$

AB \ CD	00	01	11	10
00	X	1		X
01	X			X
11	1	X		X
10		X		

For $E=1$

$$MS_1 = A'B'C' + BD'$$

So, minimum SOP expression of $F = MS_0 + E(MS_1)$
 $= A'D + BCD' + AC'D + E(A'B'C' + BD')$

Q7) Using the method of map-entered variables, use four-variable maps to find a minimum sum-of-products expression for $F(A, B, C, D, E, F, G) = \sum_m(2, 5, 6, 9) + \sum_d(1, 3, 4, 13, 14) + E(m_{11} + m_{12}) + F(m_{10}) + G(m_0)$.

Ans $\rightarrow F(A, B, C, D, E, F, G) = \sum_m(2, 5, 6, 9) + \sum_d(1, 3, 4, 13, 14) + E(m_{11} + m_{12}) + F(m_{10}) + G(m_0)$

For $E=G=F=0$,

AE \ CD	00	01	11	10
00		X	X	1
01	X	1		1
11		X		X
10		1		

$$MS_0 = C'D + A'CD'$$

For $E=F=0, G=1$

AE \ CD	00	01	11	10
00	1	X	X	X
01	X	X		X
11		X		X
10		X		

$$MS_3 = A'B'$$

+ $G(m_0)$
For $E=1, F=0, G=0$

AB \ CD	00	01	11	10
00		X	X	X
01	X	X		X
11	1	X		X
10		X	1	

$$MS_1 = BC' + B'D$$

For $E=G=0, F=1$

AB \ CD	00	01	11	10
00		X	X	X
01	X	X		X
11		X		X
10	0	X		1

$$MS_2 = CD'$$

So, minimum SOP of $F = MS_0 + E(MS_1) + F(MS_2) + G(MS_3)$
 $= C'D + A'CD' + E(BC' + B'D) + F(CD') + G(A'B')$

Q)8) Design a combinational circuit with 3 inputs X, Y & Z and one output F. The output is 1 when the binary value of the inputs is less than or equal to 2. The output is 0 otherwise.

Ans → Truth table →

Inputs			Output
X	Y	Z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


K-map →

X \ YZ	00	01	11	10
0	1	1		1
1				

$$F = X'Z' + X'Y'$$

$$= X'(Y' + Z')$$

Circuit Diagram →

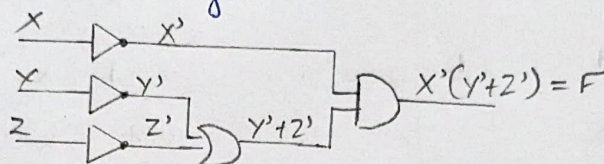

Q)9) Design a combinational circuit with four inputs A, B, C & D and one output F. The output F value is 0 if three or four of the inputs are 1; otherwise the value of F is 1.


Ans → Truth Table →

Inputs				Output
A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

K-map for F max →

AB \ CD	00	01	11	10
00				
01			0	
11		0	0	0
10			0	
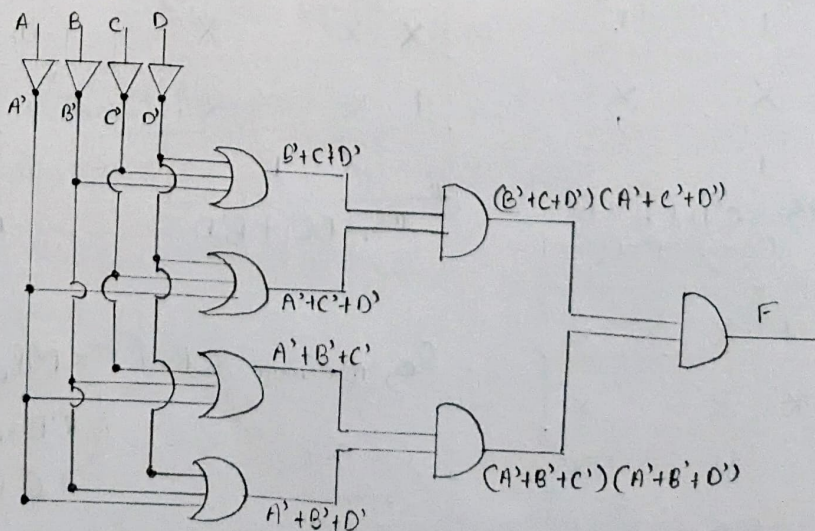
$$F_{max} = (B' + C' + D')(A' + C' + D')(A' + B' + C')(A' + B' + D')$$



Q) 10) Design a 4-bit BCD to Excess-3 code converter.

Ans → Truth table →

Inputs				Outputs			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

K-map →

For W →

AB \ CD	00	01	11	10
00				
01		1	1	1
11	x	x	x	x
10	1	1	x	x

$$W = A + BD + BC = A + B(C + D)$$

For X →

AB \ CD	00	01	11	10
00		1	1	1
01	1			
11	x	x	x	x
10		1	x	x

$$X = B'D + B'C + BC'D' \\ = B'(C + D) + BC'D'$$

For Y →

AB \ CD	00	01	11	10
00	1		1	
01	1		1	
11	x	x	x	x
10	1		x	x

$$Y = C'D' + CD \\ = C \oplus D$$

For Z →

AB \ CD	00	01	11	10
00	1		1	
01	1			1
11	x	x	x	x
10	1		x	x

$$Z = C \oplus D$$

Circuit Diagram →

